

# design ideas



The best of  
design ideas

Check it out at:  
[www.edn.com](http://www.edn.com)

Edited by Bill Travis

## Circuit provides 4- to 20-mA loop for microcontrollers


Robert Most, Dow Corning Corp, Auburn, MI

**T**HE 4- TO 20-mA current loop is ubiquitous in the world of controls in manufacturing plants. Discrete logic, microprocessors, and microcontrollers easily cover the digital portions of control schemes, such as limit switches, pushbuttons, and signal lights. Interfacing a 4- to 20-mA output to a rudimentary microcontroller can be problematic. A built-in A/D converter would be nice, but such a device is sometimes unavailable in the “economy” line of these processors. Serial 4- to 20-mA chips exist but are relatively expensive and require serial programming and involve microcontroller overhead. Most lower end chips lack dedicated serial ports and require pin-programming.

This circuit is a low-cost alternative that provides not only a 4- to 20-mA output, but also a digital feedback signal that indicates an open wire in the current loop (Figure 1). One output-port pin sets the current, and one input-port pin monitors an open circuit in the loop wire. The circuit does not require the open-loop feedback portion of the circuit for the current loop to operate; you can omit it for further cost savings.

The circuit derives its drive from a simple timer output in the microcontroller. The duty cycle of the timer determines the output current of the circuit. The input RC network in front of the first operational-amplifier signal conditions the pulse train from the processor, so that the op amp interprets it as a dc voltage. In addition, the network ensures that the minimum input voltage is close to 100 mV, even if the input is at ground potential. This minimum voltage ensures that the feedback loop of the first op amp does not fold back to the positive rail when you cut off npn transistor  $Q_1$ . If you use a dual supply, the transistor has the ad-

Figure 1

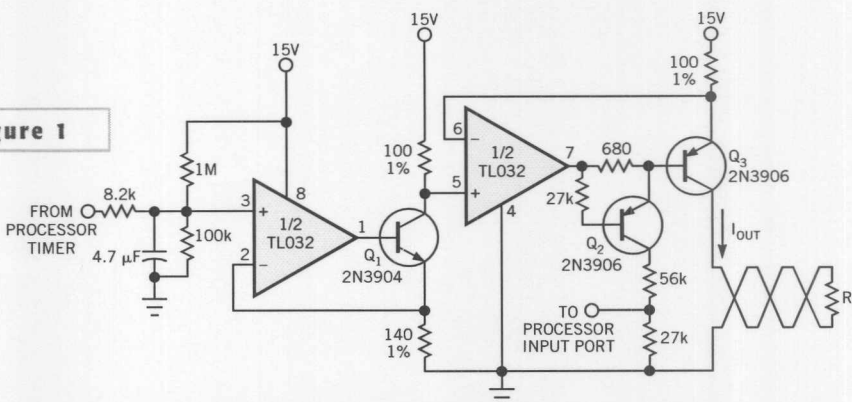

This configuration provides both a 4- to 20-mA loop and an open-circuit indication.

ditional voltage swing below ground potential to keep it in its active region and does not cut off. The emitter resistor of npn transistor  $Q_1$  sets the current span of the circuit. With a 5V drive from the microcontroller, the output current is 20 mA. A grounded input results in less than 1 mA. A duty cycle of 12.5% drives the loop at 4 mA and exhibits linear control to full scale. Although it may not be mandatory, most current loops prefer a grounded return path. The purpose of the second operational amplifier is to provide a current source, rather than the current sink of the first stage, and the grounded return path. Hence, pnp transistor  $Q_3$  provides this high-side drive. Bipolar-junction transistors  $Q_1$  and  $Q_3$  meet cost considerations, but you could also use MOSFETs for slightly better performance.

The open-loop feedback portion of this circuit lets the microcontroller know that a fault condition exists on the line. The processor can then execute alarm, shutdown, or other control functions to mitigate possible safety concerns. When an open-loop condition occurs,  $Q_3$  shunts the entire loop current

back through its emitter-base junction and through the 680Ω resistor to the op amp. The voltage developed across the 680Ω resistor turns on  $Q_2$ , resulting in a logic-one feedback to the microcontroller. Note that the open loop requires at least 1 mA of current for the open indication to function, which is below the normal 4 mA—a “zero” output condi-

Circuit provides 4- to 20-mA loop for microcontrollers.....	89
Minimize the short-circuit current pulse in a hot-swap controller .....	90
Reduce EMI by sweeping a power supply's frequency .....	92
Get just enough boost voltage .....	94
Processor's PWM output controls LCD/LED driver .....	96
Method provides automatic machine shutdown .....	98
Circuit makes simple high-voltage inverter .....	100

Publish your Design Idea in EDN. See the What's Up section at [www.edn.com](http://www.edn.com).

tion for this type of control system.

Response time for a step change is approximately 500 msec, which is acceptable for most current-loop control devices, such as control valves. If the

microcontroller you select has a built-in A/D converter, response time can decrease by a couple of orders of magnitude with the elimination of the input-filtering network. Op-amp selec-


tion is important if you use a single-supply topology. An operational amplifier that can maintain stability close to its negative, or ground, rail is an important asset. □

## Minimize the short-circuit current pulse in a hot-swap controller

Jim Sherwin and Thong Huynh, Maxim Integrated Products, Sunnyvale, CA

**B**ECAUSE OF INTERNAL circuit-breaker delay and limited MOS-gate pulldown current, many hot-swap controllers do not limit current during the first 10 to 50  $\mu$ sec following a shorted output. The result can be a brief flow of several hundred amperes. A simple external circuit can counter this problem by minimizing the initial current spike and terminating the short circuit within 200 to 500 nsec. A

typical 12V, 6A, hot-swap-controller circuit contains, as do many others, slow and fast comparators with trip thresholds of 50 and 200 mV (Figure 1). The 6-m $\Omega$  sense resistor,  $R_S$ , allows a nominal slow-comparator trip at 8.3A for overload conditions and a fast-comparator trip at 33.3A for short circuits. Only circuit resistances limit the initial short-circuit current spike during a period that includes the fast-comparator delay and the 30  $\mu$ sec it takes to complete interruption of the short circuit by discharging  $M_1$ 's gate capacitance. Various elements, such as  $R_S$  and the on-resistance of  $M_1$ , contribute to the circuit

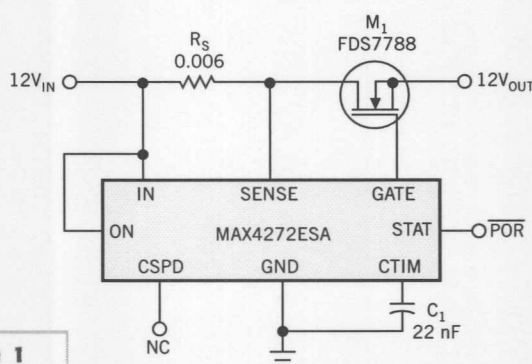

**Figure 1**


A typical hot-swap controller circuit exhibits a 30- $\mu$ sec short-circuit current pulse of 400A peak.

resistances. The waveform recorded during a short circuit indicates a peak current of 400 from the 2.4V peak across  $R_S$ , decreasing to 100A in 28  $\mu$ sec (Figure 2).

You can limit the short-circuit current duration to less than 0.5  $\mu$ sec by adding a Darlington pnp transistor,  $Q_1$ , to speed the gate discharge (Figure 3).  $D_1$  allows the gate to charge normally at turn-on, but, at turn-off, the controller's 3-mA gate-discharge current is directed to the base of  $Q_1$ .  $Q_1$  then acts quickly to discharge the gate, in less than 100 nsec. Thus, the high-current portion of the short circuit is limited to slightly more than the fast comparator's delay time of 350 nsec. The apparent reverse overshoot current and the steep rise in the waveform of Figure 4 arise from


parasitic series inductance in the sense-resistor chip.  $C_2$  connects between the gate and source of  $M_1$  to reduce the positive-transient step voltage applied to the gate during a short circuit. Zener diode  $D_1$  reduces  $I_{D(ON)}$  by limiting  $V_{GS}$  to less than the 7V available from the MAX4272. Although  $D_1$

The oscilloscope's ground lead introduces an artifact, which appears as the leading-edge oscillation in Figure 6. Again, as in Figure 4, the apparent reverse-overshoot current and the steep rise in the waveform of Figure 6 arise from parasitic series inductance in the sense-resistor chip.  $C_2$  connects between the gate and source of  $M_1$  to reduce the positive-transient step voltage applied to the gate during a short circuit. Zener diode  $D_1$  reduces  $I_{D(ON)}$  by limiting  $V_{GS}$  to less than the 7V available from the MAX4272. Although  $D_1$

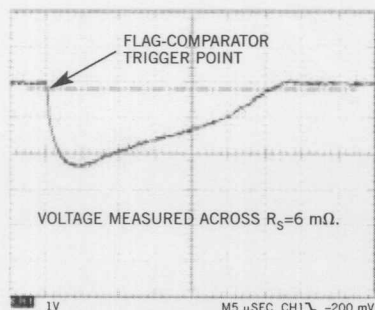

**Figure 2**

The short-circuit current in Figure 1 is 400A, decreasing to 100A in 28  $\mu$ sec.

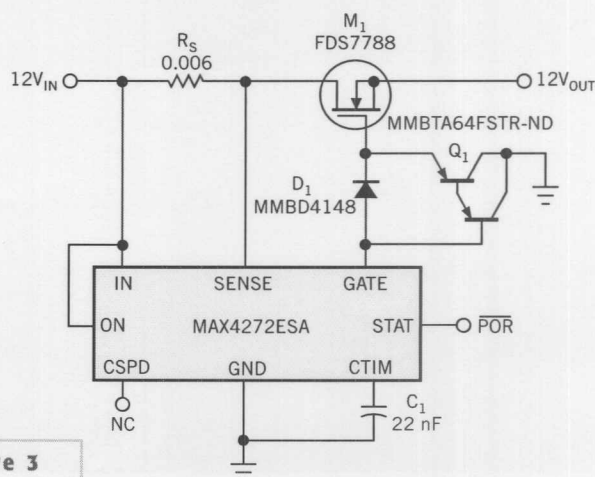

**Figure 3**

The addition of  $Q_1$  increases the gate-pulldown current, limiting the short-circuit-current duration to less than 0.5  $\mu$ sec.